

## WECHSELSTROM

$$1) \quad Z = \sqrt{R^2 + (\omega L)^2} \quad \text{und} \quad \tan \varphi = \frac{\omega L}{R} \quad \Rightarrow \quad L = \frac{R \tan \varphi}{\omega}$$
$$= \sqrt{R^2 + R^2 \tan^2 \varphi}$$

$$\hat{I} = \frac{U}{Z} = \frac{U}{R \sqrt{1 + \tan^2 \varphi}} = \frac{\sqrt{2} \cdot 230 \text{ V}}{30 \Omega \cdot \sqrt{1 + \tan^2 55^\circ}} = 6,2 \text{ A}$$

$$2) a) \quad L = \frac{\mu_0 N^2 A}{l} = \frac{4\pi \cdot 10^{-7} \frac{\text{Vs}}{\text{Am}} \cdot 1000^2 \cdot \pi (0,015 \text{ m})^2}{10 \text{ m}} = 0,89 \text{ mH}$$

$$b) \quad I = \frac{U}{Z} = \frac{U}{\sqrt{R^2 + (\omega L)^2}} = \frac{U}{\sqrt{R^2 + \frac{4\pi^2 f^2 \mu_0^2 N^4 \pi^2 r^4}{l^2}}}$$

$$= \frac{230 \text{ V}}{\sqrt{(20 \Omega)^2 + \frac{4\pi^2 (350 \text{ kHz})^2 \cdot 1000^2 \cdot 4\pi \cdot 10^{-7} \frac{\text{Vs}}{\text{Am}} \cdot \pi^2 (0,015 \text{ m})^2}{(10 \text{ m})^2}}} = 1,0 \text{ A}$$

$$c) \quad \varphi = \arctan \frac{\omega L}{R} = \arctan \frac{2\pi f \cdot \mu_0 N^2 \pi r^2}{l R}$$
$$= \arctan \left( \frac{2\pi \cdot 350 \text{ kHz} \cdot 4\pi \cdot 10^{-7} \frac{\text{Vs}}{\text{Am}} \cdot 1000^2 \cdot \pi (0,015 \text{ m})^2}{10 \text{ m} \cdot 20 \Omega} \right) = 44,3^\circ$$

$$d) \quad P_1 = \frac{U^2}{R} = I_2^2 \cdot R = \frac{U^2 R}{R^2 + \frac{4\pi^2 f^2 \mu_0^2 N^4 \pi^2 r^4}{l^2}} = \dots = 2100 \text{ W}$$

$$P_2 = U \cdot I \cdot \cos \varphi = \frac{U^2 \cdot \cos \arctan \left( \frac{2\pi R \mu_0 N^2 \pi r^2}{l R} \right)}{\sqrt{R^2 + \frac{4\pi^2 f^2 \mu_0^2 N^4 \pi^2 r^4}{l^2}}} = \dots = 2,00 \text{ W}$$

$$3) \quad f_1 = 2 \text{ kHz} \quad R = 10 \Omega$$
$$I_1 = 78 \text{ mA} \quad U = 8 \text{ V}$$
$$\varphi_2 = 45^\circ$$
$$I = \frac{U}{Z} = \frac{U}{\sqrt{R^2 + (\omega L)^2}} \Rightarrow L = \frac{1}{2\pi f_1} \sqrt{\left(\frac{U}{I}\right)^2 - R^2}$$

$$\tan \varphi_2 = \frac{\omega L}{R} \quad L = \frac{R \tan \varphi}{2\pi f_2}$$

$$\frac{R \tan \varphi_2}{2\pi f_2} = \frac{1}{2\pi f_1} \sqrt{\frac{U^2}{I^2} - R^2}$$

$$f_2 = \frac{f_1 R \tan \varphi_2}{\sqrt{\frac{U^2}{I^2} - R^2}} = \frac{2 \text{ kHz} \cdot 10 \Omega \cdot 1}{\sqrt{\left(\frac{8V}{0,03A}\right)^2 - (10 \Omega)^2}} = 196 \text{ Hz}$$

$$4) a) Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{(5,8 \Omega)^2 + \left(2\pi \cdot 4500 \frac{1}{s} \cdot 0,0031 \text{ H} - \left(2\pi \cdot 4500 \frac{1}{s} \cdot 0,37 \mu\text{F}\right)^{-1}\right)^2}$$

$$= 9,8 \Omega$$

$$b) I_{\text{eff}} = \frac{U}{Z} = \frac{U}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \dots = 0,75 \text{ A}$$

$$\hat{I} = \frac{U}{Z} \sqrt{2} = \frac{U\sqrt{2}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \dots = 1,1 \text{ A}$$

$$c) \varphi = \arctan \frac{\omega L - \frac{1}{\omega C}}{R} = \arctan \frac{2\pi \cdot 4500 \frac{1}{s} \cdot 31 \text{ mH} - \left(2\pi \cdot 4500 \frac{1}{s} \cdot 0,37 \mu\text{F}\right)^{-1}}{5,8 \Omega}$$

$$= -53,8^\circ = -0,94 \text{ rad}$$

$$d) S = U \cdot I = \frac{U^2}{Z} = \frac{U^2}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \dots = 5,6 \text{ VA}$$

$$Q = U \cdot I \cdot \sin \varphi = \frac{U^2}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \sin \left( \arctan \frac{\omega L - \frac{1}{\omega C}}{R} \right) = \dots = 4,5 \text{ VAR}$$

$$P = U \cdot I \cdot \cos \varphi = \frac{U^2}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \cos \left( \arctan \frac{\omega L - \frac{1}{\omega C}}{R} \right) = \dots = 3,3 \text{ W}$$


$$e) \text{ Wirkleistung } P = U_R \cdot I_R = R \cdot I^2 = R \cdot \frac{U^2}{Z^2} = \frac{R \cdot U^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \dots = 3,3 \text{ W}$$

$$f) I_{\text{max}} \Leftrightarrow Z_{\text{min}} \Leftrightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow 4\pi^2 f^2 = \frac{1}{LC} \quad f = \sqrt{\frac{1}{4\pi^2 LC}} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{31 \text{ mH} \cdot 0,37 \mu\text{F}}} = 4,7 \text{ kHz}$$

$$g) I = \frac{U}{Z_{\text{min}}} = \frac{U}{R} = \frac{7,4 \text{ V}}{5,8 \Omega} = 1,3 \text{ A}$$

6) a)

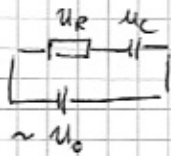

$$U_C = \sqrt{U_0^2 - U_R^2} \quad (\text{Pythagoras}) \quad U_C = Z_C \cdot I$$

$$P_R = U_R \cdot I_R = U_R \cdot I = \frac{U_R^2}{R} = \frac{I^2}{\omega C}$$

$$C = \frac{I}{\omega U_C} = \frac{I}{2\pi f \sqrt{U_0^2 - U_R^2}} = \frac{P_R}{2\pi f U_R \sqrt{U_0^2 - U_R^2}}$$

$$= \frac{40W}{2\pi \cdot 50 \frac{1}{s} \cdot 110V \sqrt{(230V)^2 - (110V)^2}} = 5,7 \mu F$$

$$Q = U \cdot I \cdot \sin \varphi = U \cdot I \cdot \sin \left( \arctan \frac{1/\omega C}{R} \right) =$$

$$= \frac{U_0^2}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \cdot \sin \left( \arctan \frac{U_C}{U_R} \right) = \frac{U_0^2}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \sin \arctan \left( \frac{\sqrt{U_0^2 - U_R^2}}{U_R} \right) =$$

$$= \frac{(110)^2}{\sqrt{\left(\frac{40^2}{P_R}\right)^2 + \left(\frac{110 \sqrt{U_0^2 - U_R^2}}{P_R}\right)^2}} \cdot \sin \left( \arctan \frac{\sqrt{U_0^2 - U_R^2}}{U_R} \right) = \dots = 73W$$

5) b)  $P = U_p \cdot I = 104,5V \cdot 0,455A = 47,5W$

c) sollte nach Pythagoras addiert werden.

$$\sqrt{U_R^2 + U_L^2} = \sqrt{(104,5V)^2 + (174,3V)^2} = 203,2V < 224,3V$$

 $\Rightarrow$  Innenwiderstand der Drossel nicht vernachlässigbar klein.

$$d) \varphi = \arctan \frac{U_L}{U_R} = \arctan \frac{174,3V}{104,5V} = 1,031 \text{ rad}$$

$$\approx \arctan \frac{\sqrt{U_0^2 - U_R^2}}{U_R} = \arctan \frac{\sqrt{(224,3V)^2 - (104,5V)^2}}{104,5V} = 1,056 \text{ rad}$$

$$\approx \arctan \frac{U_L}{\sqrt{U_0^2 - U_R^2}} = \arctan \frac{174,3V}{\sqrt{(224,3V)^2 - (174,3V)^2}} = 0,890 \text{ rad}$$

$$e) \omega L = \frac{U_L}{U_R} \quad L = \frac{R U_L}{2\pi f U_R} = \frac{U_R U_L}{2\pi f I U_R} = \frac{U_L}{2\pi f I} \approx \frac{174,3V}{2\pi \cdot 50Hz \cdot 0,455A} = 1,22H$$

$$R = \frac{U_R}{I}$$

$$L \approx \frac{\sqrt{U_0^2 - U_R^2}}{2\pi f I} = \frac{\sqrt{(224,3V)^2 - (104,5V)^2}}{2\pi \cdot 50Hz \cdot 0,455A} = 1,39H$$